

Experiment #3 – Function Generator

Student Name: Marzieh Bagheri Nia Amiri

Student ID: 810197682

First Part: Design Waveform Generator

1. As stated in instruction, I wrote a Verilog code and test it in Modelsim. The waveform of all 7 functions can be seen in the following picture.

 


Figure 1

- A clearer picture of Figure1 exists in LAB3 \ WaveformGenerator\ Modelsim folder.
- All the above project exists in LAB3\WaveformGenerator\ Modelsim folder.

2, 3. Then we put the written code in Quartus and then we add the 1-port ROM to it; So our waveform Generator is ready. The block diagram of waveform generator can be seen below:

 


Figure 2

- A clearer picture of Figure2 exists in LAB3 \ Waveform Generator\ Quartus folder.

4. In this section, I write a testbench for my circuit and test it in Modelsim. The waveform of ROM's output can be seen below:

- A clearer picture of Figure3 exists in LAB3 \ WaveformGenerator\ Quartus folder.
- All the above project exists in LAB3\WaveformGenerator\ Quartus folder.

 


Figure 3

Second Part: Design Frequency Regulator

● In last Experiment, I could not complete this section properly, so I used the second method, which was said to be permissible to use. At first, I test my design in Modelsim. In this test, I turned the clock that came out of the ring oscillator into a pulse with 50MHz frequency ($T = 20\text{ns}$). The result of this test can be seen below:

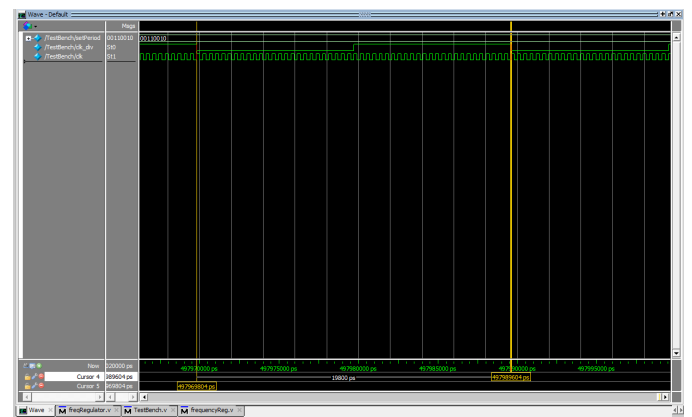


Figure 4

- A clearer picture of Figure4 exists in LAB3 \ FrequencyRegulator\Modelsim folder.
- All the above project exists in LAB3 \ FrequencyRegulator \Modelsim folder.

1. In this section, we add the FrequencyRegulator to waveform Generator and then we synthesize the whole circuit. The block diagram of waveform generator + frequency selector can be seen below:

 


Figure 5

- A clearer picture of Figure5 exists in LAB3\FunctionGenerator\FreqPlusWaveGen folder.

All the above project exists in LAB3\FunctionGenerator\FreqPlusWaveGen folder.

2. I write a simple testbench for this circuit and test it in modelsim with 3 different setPeriods. The following pictures show the result of these three different values:

setPeriod	Achieved Freq	Figure number
25	8MHz	6
50	4MHz	7
100	2MHz	8

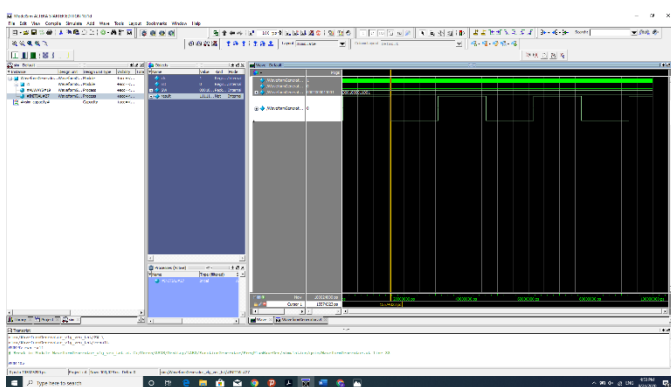


Figure 6

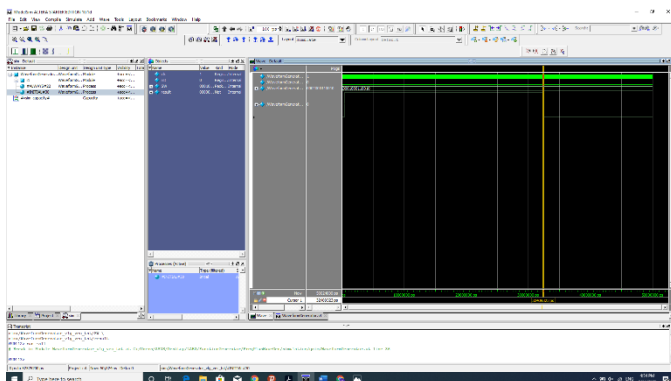


Figure 7

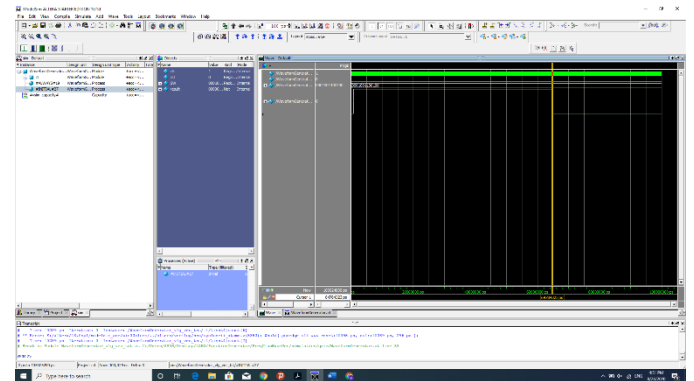


Figure 8

- A clearer pictures of Figure6, Figure7, Figure8 exist in LAB3\FunctionGenerator\FreqPlusWaveGen folder.

Third Part: Design Amplitude Selector

In this part, I write a Verilog code for Amplitude Selector and then test it with a simple testbench in Modelsim. The result can be seen below:

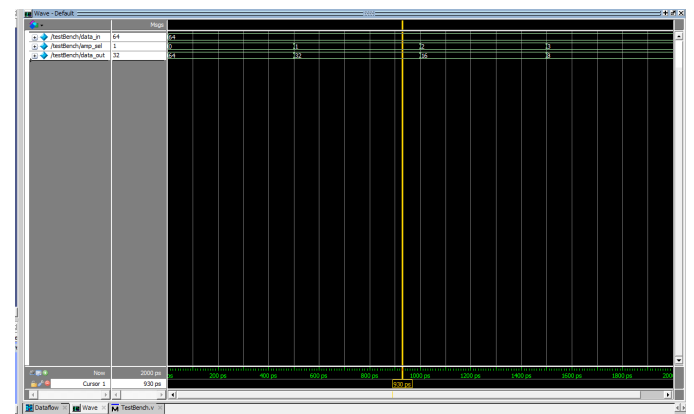


Figure 9

- A clearer picture of Figure9 exists in LAB3 \ AmplitudeSelector folder.

All the above project exists in LAB3 \ AmplitudeSelector folder.

Forth Part: Design Whole project

1. At first we combine Waveform generator, Frequency Selector and Amplitude Selector together. The block diagram of top_level design can be seen below:

 


Figure 10

- A clearer picture of Figure10 exists in LAB3\FunctionGenerator \FunctionGenerator folder.

2. We write a simple testbench for design and test it in Modelsim. The following pictures show two examples of tests performed on the design:

Function	Amplitude Select	Figure number
Square	01	11
Sine	10	12

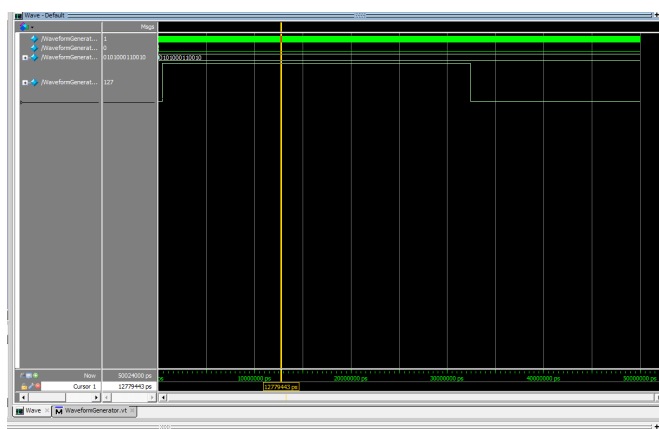


Figure 11

- A clearer picture of Figure11 exists in LAB3\FunctionGenerator \FunctionGenerator folder.

 


Figure 12

- A clearer picture of Figure12 exists in LAB3\FunctionGenerator \FunctionGenerator folder.